

# Breadboard Power Supply

**Timothy Leishman**

*Senior Instructor, Robotics Engineering Technology  
Idaho State University*

# Contents

- Section 1 Introduction 2
- Section 2 RMS & Peak Voltage 4
- Section 3 Voltage Rectification 5
- Section 4 Capacitive Filtering & DC Calculations 7
- Section 5 Voltage Regulation 9
- Section 6 Your First Power Supply Project 13
- Section 7 Zener Regulation 16
- Section 8 Input Polarity Correction 20
- Section 9 Basic Current Limiting Protection 21
- Section 10 The Darlington Pair 24
- Section 11 The L7805 Regulator 26
- Section 12 Breadboard Power Supply Assembly 29
- Conclusion 32
- References 33

## Section 1 Introduction

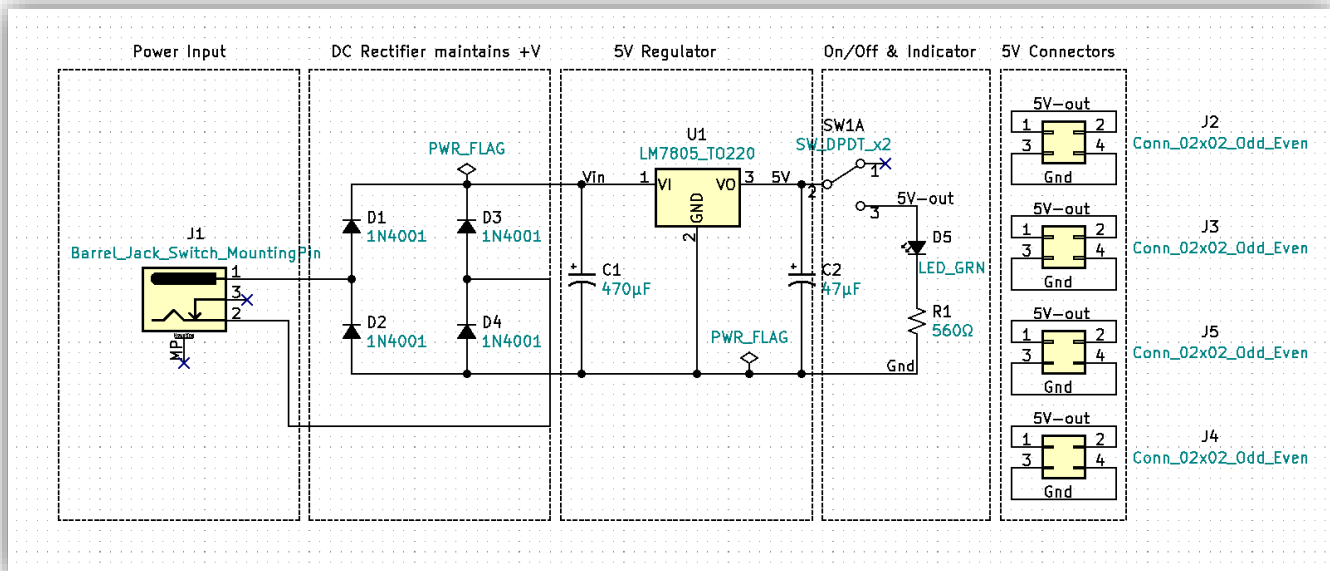


Figure 1-1 Breadboard Power Supply Schematic

In addition to a global pandemic, Covid created an instant demand for online at home learning. Suddenly electronics students everywhere lost access to Laboratory Bench Test Equipment and the direct supervision of a Lab Instructor. Modestly priced oscilloscopes, function generators, and laboratory DC power supplies exist and I encourage advanced students to acquire these tools as they can. However, the introductory student will not likely have access to these tools at home and for them the Breadboard PS along with a DMM will provide an affordable and safe, at home circuit prototyping solution.

The electronic circuit design process involves defining a problem, determining a solution, circuit calculations & schematic development, acquiring the needed components, circuit testing (often referred to as breadboarding), PCB or printed circuit board


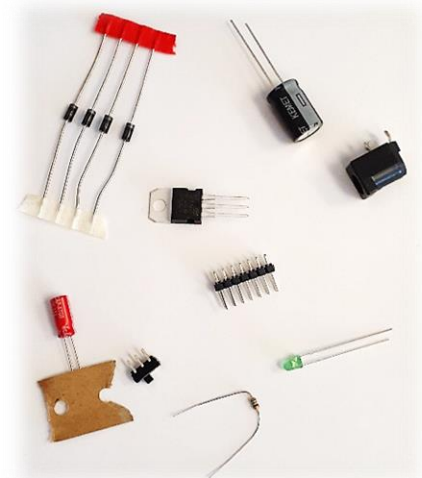


Figure 1-2 Electronic Components

development, PCB assembly, and final testing. Typically, the breadboarding stage is done using a bench top or Laboratory DC Power Supply. Once the breadboarding phase is complete and the circuit is functionally operational, we often need to replace the laboratory DC power supply with a dedicated power source. A power source can be as simple as a 9V battery or may be a dedicated high-power rackmount subsystem. Often, we can design our own power supplies using basic components rather than buying the off the shelf unit.

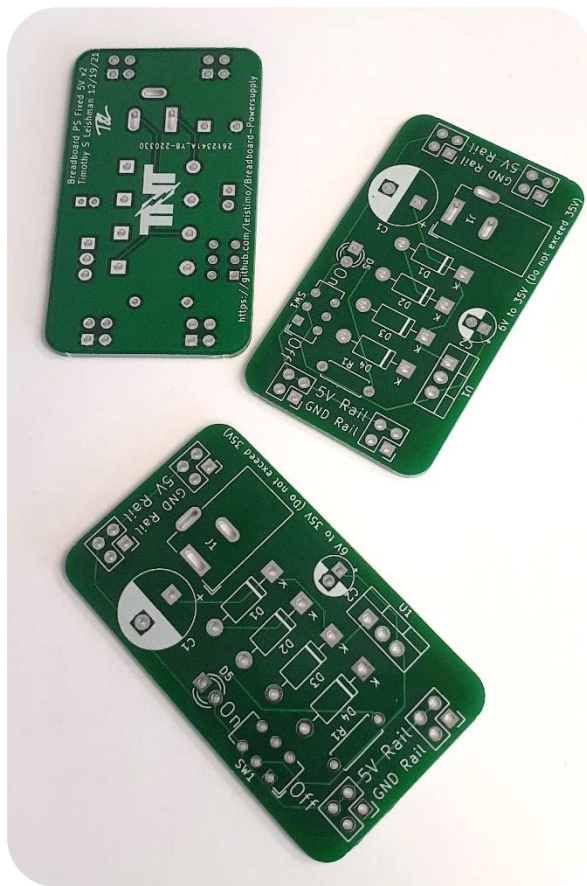

**Figure 1-3** Printed Circuit Boards (PCBs)

While the power supply may not be the most exciting aspect of your electronic projects it is a crucial and foundational component. Poor power supply design can lead to intermittent circuit problems, premature circuit failures, and frustration! Understanding how power supplies operate and function will make you a better electronic troubleshooter. The Breadboard Power Supply will give you the ability to safely build and test circuits. This small project will also help you develop your soldering skills. Additionally, learning how to safely design and build dedicated power supplies will bring life to your current and future electronic projects.

## Section 2 RMS & Peak Voltage

The wall outlet at your house is 120-volt rms. 120vrms is dangerous. The circuit breaker at your house, which acts like a safety switch turning off the voltage, has the maximum current rating of 15 amps to 20 amps. Death can occur from as low as 100mA or 0.1A. The circuit breaker at your house is not designed to save your life from electrical shock, it is designed to prevent the wiring in your home from overheating heating and starting a fire. Do not mess 120v wall power it can kill you! For more safety information, here is a link to [OSHA's Basic Electrical Safety](#).

Wall voltage is known as AC (Alternating Current). Most of what we do in electronics is DC (Direct Current). Examples of DC devices include: your computer, cell phone, Arduino, Raspberry Pi, and anything powered by a battery. The motor in your RC car is DC motor. However, some motors are designed to operate using single phase AC or industrial three phase AC. Because our wall power is AC and our electronic circuits are predominately DC we will need to convert the alternating wall current to direct current. The process of converting AC to DC is called Rectification.

Figure 2-1 shows a captured image of 120vRMS wall AC. An Oscilloscope displays voltage along the Y axis and time along the X axis. Observe that the Oscilloscope displays the image in alternating peak to peak voltage not RMS voltage.

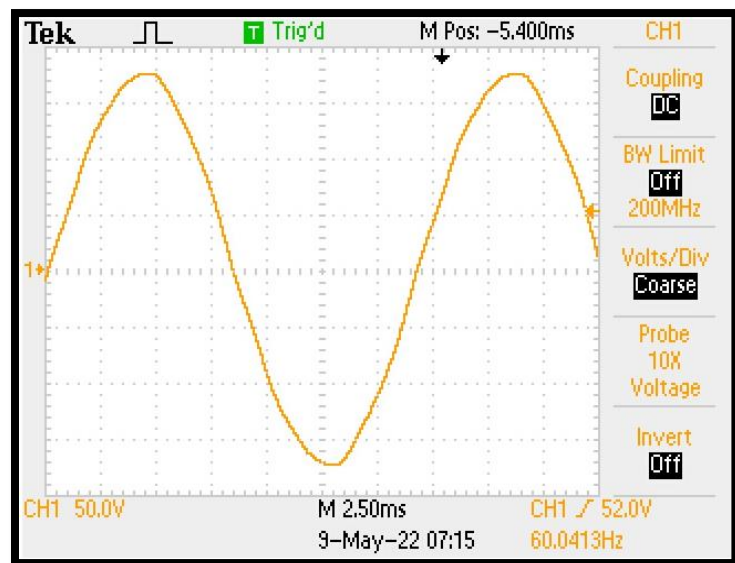


Figure 2-1 120vrms waveform on oscilloscope

To convert peak to peak voltage to RMS voltage, the following formulas can be used.

$$V_{rms} = \frac{V_p}{\sqrt{2}} \text{ OR } V_p \times 0.707. V_p \text{ is peak voltage and is equal to } V_{pp} \text{ (peak to peak voltage)}$$

divided by two or  $V_p = \frac{V_{pp}}{2}$ . In figure 2-1 note that channel 1 is set to 50 volts per division and the waveform, peak to peak, has approximately six major divisions and two half divisions equaling 7 major divisions. Now if we multiply  $7div \times 50v/div$  to get a peak to peak voltage of  $350v_{pp}$ . Dividing  $350v_{pp}$  by 2 gives us a peak voltage of  $175v_p$ . Dividing  $175v_p$  by  $\sqrt{2}$  gives an RMS voltage of  $123.74v_{RMS}$  or  $120v_{RMS}$ . Peak voltage is important to understand when we are using an oscilloscope and calculating rectification circuits. RMS is useful for determining power. For example, the power calculations for an incandescent light bulb, audio amplifier, and ac motor need to be calculated by multiplying the RMS voltage by the RMS current. Using RMS voltage to calculate ac power gives us an equivalent power to DC power calculations. Meaning  $1v_{rms} \times 1amp_{rms} = 1 watt$  &  $1VDC \times 1amp_{DC} = 1 watt$ . 1 watt is the energy needed for both scenarios.

### Section 3 Voltage Rectification

Voltage rectification is the process of changing AC (alternating current) to DC (direct current). Knowing that 100mA of current can be lethal and that in-general, skin resistance of a human is between  $10K\Omega$  &  $1K\Omega$  ( $1K\Omega$  when wet), we can use Ohm's Law, where  $Current = \frac{Voltage}{Resistance}$ , to determine a relatively safe voltage. If we convert  $120v_{rms}$  to peak we get  $v_p = 120V \times \sqrt{2}$  or  $v_p = 169.71v_p$ . Now assuming we were able to rectify the 169.71volts we can use the human resistance of  $1K\Omega$  to determine the current potential,  $i_{amps} = \frac{169.71V}{1000\Omega}$ ,  $i =$

169.71mA. This current is potentially lethal. If 100mA is our threshold for lethal current. What is the maximum “safe” voltage?

Calculate the max voltage by  $V_{max} = 1K\Omega \times 100mA$ ,  $V_{max} = 100v$ . Now we know that 100Vs and above is potentially lethal

for humans, less than 100V should be

less than lethal. Figure 3-1 shows a

basic unregulated half-wave voltage

rectifier circuit, transformer T1 is

used for isolation and safety. Notice

that T1 has a 4:1 turns ratio. T1 is a

step-down transformer meaning that the

primary side (pins 1 & 2) have four times more turns than the secondary side (pins 3 & 4). A

step-down transformer’s secondary voltage will be divided by the turns’ ratio. For a 4:1

transformer,  $v_{secondary} = \frac{V_{primary}}{4} = \frac{169.71vp}{4} = 42.43vp$ . Figure 3-2 shows the secondary

voltage waveform of T1 pin 3 to pin 4.

The voltage has been stepped down to around 42vp. The waveform however, is still AC. Observe the frequency for both fig 2-1 and fig 3-2. Frequency is measured in hertz (Hz) and both the primary and the secondary are measuring the same frequency at 60Hz which is the standard frequency for AC power in the United States.

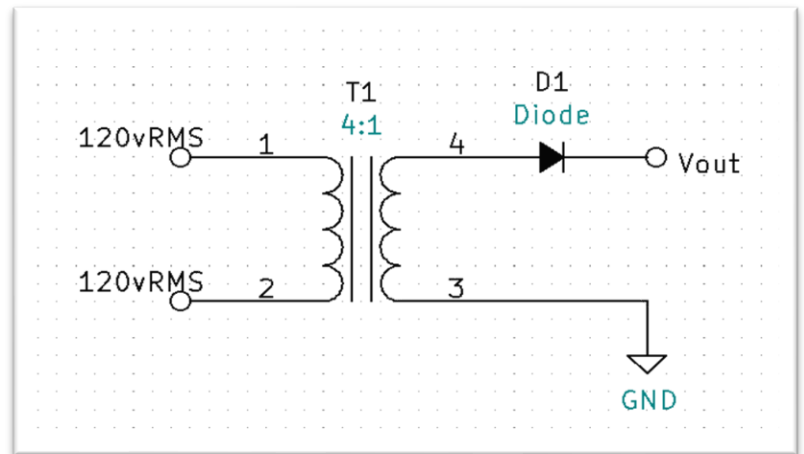


Figure 3-1 Basic Half Wave Rectifier Circuit

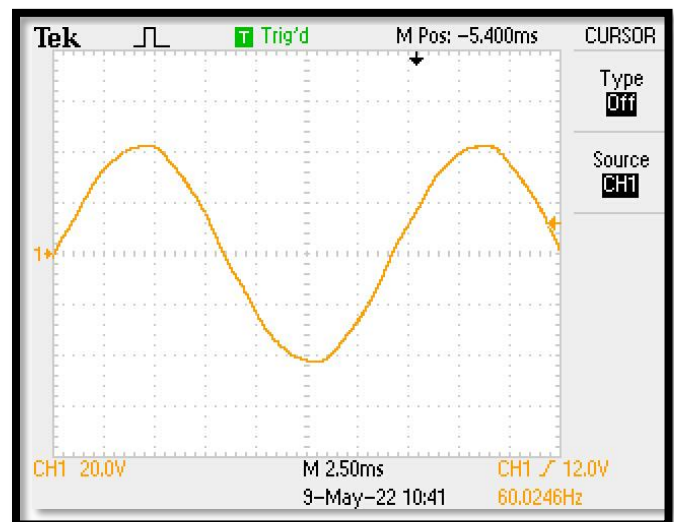


Figure 3-2 Secondary Waveform Voltage of 4:1 Transformer



The diode D1 of Figure 3-1 will provide rectification by acting like a switch and allowing

current to flow in only one direction. When the anode is positive with respect to the cathode, current will flow.

When the anode is negative with respect to the cathode

the diode will act like an open and no current will flow.

Figure 3-3 diode anode and cathode

The output waveform will now appear to have the negative peaks clipped off (See fig 3-4). The current is flowing in one direction and basic half-wave rectification has been achieved. Notice the waveform frequency is still 60Hz for half-wave rectification.

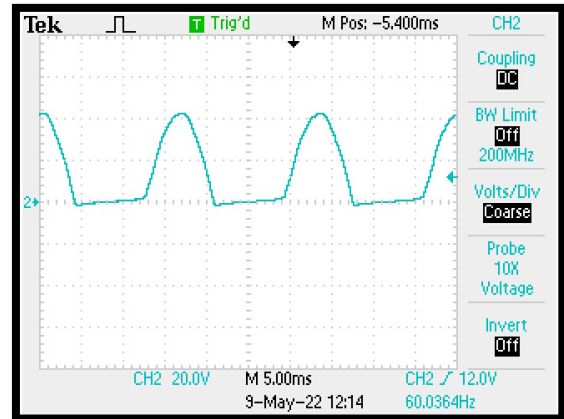


Figure 3-4 half-wave rectification

## Section 4 Capacitive Filtering & DC Calculations

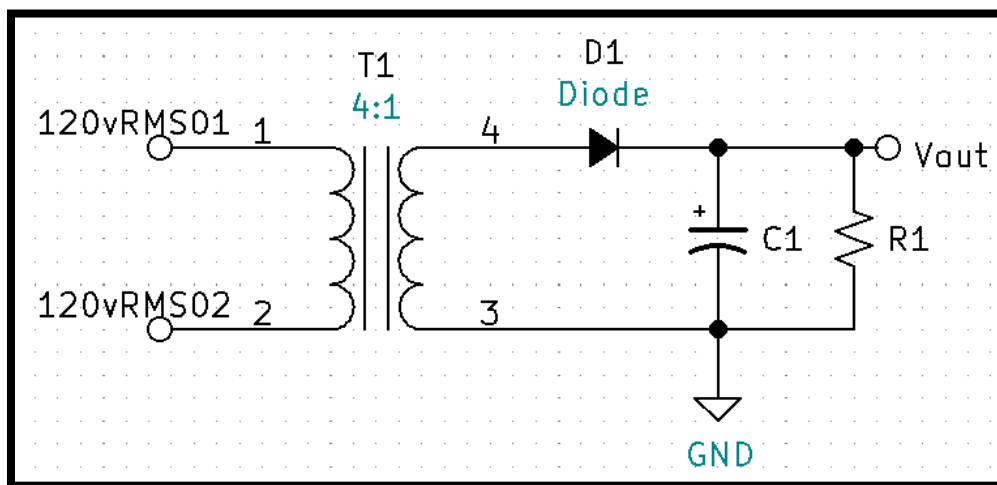


Figure 4-1 basic unregulated rectifier with filtering

By adding a filtering capacitor, we can smooth the ripple waveform to make it a better DC. Figure 4-1 has added a filter capacitor C1 in parallel with load resistor R1. The



capacitor will charge immediately when the diode D1 is forward biased. When the diode becomes reverse biased the capacitor will discharge through the load R1. With a large enough capacitance value and load resistor the output will be a smooth DC. We can test this by using a 10uF capacitor with no load, a 10KΩ load, and a 1KΩ load to show the varying degrees of ripple (see figures 4-2,4-3, & 4-4).

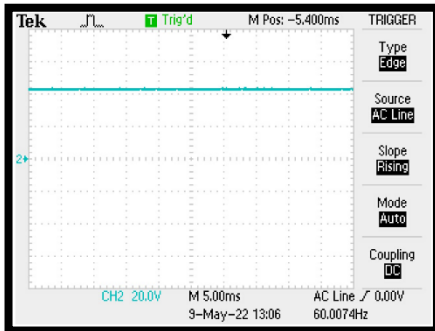


Figure 4-2 no load

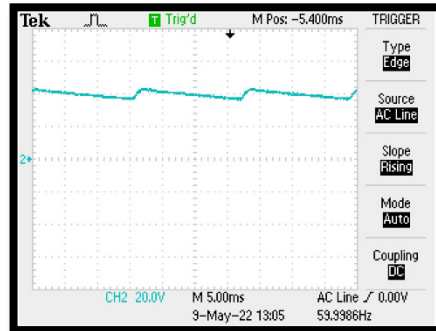


Figure 4-3 10K ohm load

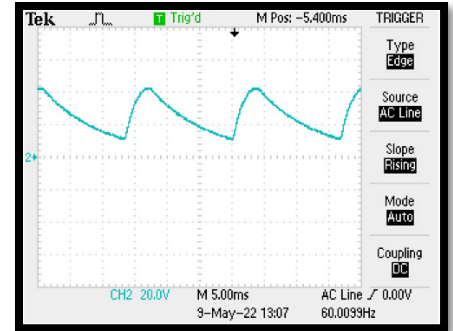


Figure 4-4 1K ohm load

When there is ripple present on the waveform, VDC can be thought of as the average waveform voltage. VDC can be calculated by adding the maximum positive peak voltage to the minimum peak voltage and then dividing the sum by two.

Example Calculate  $V_{DC}$  for figure 4-4:

$$V_{DC} = \frac{V_{max} + V_{min}}{2}$$

$$V_{max} = 2.1 \text{ div} \times 20\text{v/div} = 42\text{v}$$

$$V_{min} = 0.5 \text{ div} \times 20\text{v/div} = 10\text{v}. \text{ Now find } V_{DC}.$$

$$V_{DC_{1K\Omega}} = \frac{V_{max} + V_{min}}{2} = \frac{42\text{v} + 10\text{v}}{2} = 26\text{V}.$$

## Section 5 Voltage Regulation

For Figures 4-2, 4-3, & 4-4 observe that as the load is increased, (Ohm's law  $I = \frac{V}{R}$ , current or "load" increases as resistance is decreased), the ripple voltage increases and as the ripple increases the effective DC voltage decreases.

This is an example of a rectifier circuit that is Un-Regulated. An un-regulated power supply's DC voltage will decrease as the circuit load current is increased.

For many circuits having an unregulated power supply is a problem. Voltage regulation is required for any circuit that requires smooth consistent DC voltage across varying loads or current demands. Figure 5-1

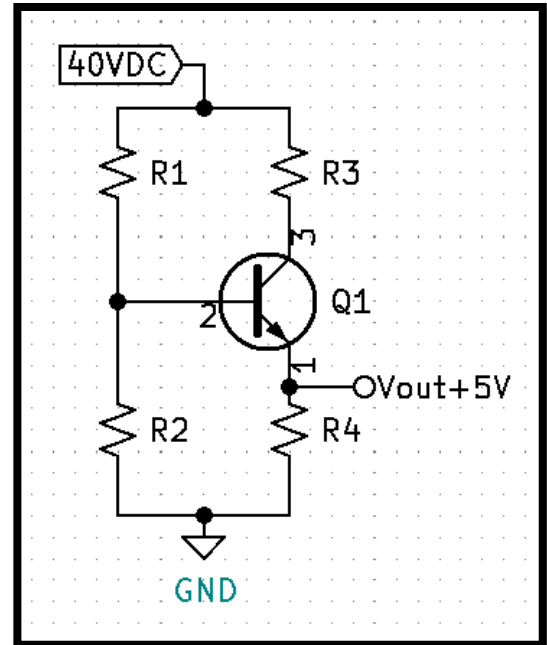


Figure 5-1 Basic Voltage Regulation Circuit

shows a common collector amplifier which can be used to provide basic voltage regulation. To calculate the needed resistors R1 thru R4, an output voltage must be determined. Next, determine the maximum current need for your circuit. For this example, we will use 5V with a maximum current need of 5mA. Calculate the base current (pin 2) of the transistor by dividing the 5mA emitter current (pin 1) by the minimum beta (also known as hfe) per the data sheet. The minimum hfe for the 2N3904 with a collector current near 5mA will be will be between 80 and 100, see figure 5-2.

- $I_B \approx \frac{5mA}{90} \approx 55.556\mu A$

$h_{FE}^*$	DC Current Gain	$I_C = 0.1 \text{ mA}$	$V_{CE} = 1 \text{ V}$	60			
		$I_C = 1 \text{ mA}$	$V_{CE} = 1 \text{ V}$	80			
		$I_C = 10 \text{ mA}$	$V_{CE} = 1 \text{ V}$	100		300	
		$I_C = 50 \text{ mA}$	$V_{CE} = 1 \text{ V}$	60			
		$I_C = 100 \text{ mA}$	$V_{CE} = 1 \text{ V}$	30			

Figure 5-2 beta for a 2n3904 transistor

With  $I_B$  known, make  $I_{R2}$  a minimum of 10 times larger.

- $I_{R2} \geq (10 \times I_B) \geq (10 \times 55.556\mu A) \geq 555.556\mu A$

Use Kirchhoff's Voltage Law to calculate  $V_{R2}$ .

- $V_{R2} = V_{R4} + V_{BE} = 5V + 0.7V = 5.7V$

Use Ohm's Law to calculate  $R2$

- $R_2 = \frac{V_{R2}}{I_{R2}} = \frac{5.7V}{min555.556\mu A} = 10.26K\Omega$
- Round down to next standard value,  $R_2 = 10K\Omega$

Recalculate  $I_{R2}$  using standard value.

- $I_{R2} = \frac{V_{R2}}{R_2} = \frac{5.7V}{10K\Omega} = 570\mu A$

Calculate  $I_{R1}$  using Kirchhoff's Current Law.

- $I_{R1} = I_B + I_{R2} = 55.556\mu A + 570\mu A = 625.556\mu A$

Calculate  $V_{R1}$  using Kirchhoff's Current Law.

- $V_{R1} = V_{CC} - V_{R2} = 40V - 5.7V = 34.3V$

Calculate  $R1$  using Ohm's Law.

- $R_1 = \frac{V_{R1}}{I_{R1}} = \frac{34.3V}{625.556\mu A} = 54.831K\Omega$

$R3$  is used to help split the power from the transistor. Power for the transistor is calculated using the max current  $I_C$  multiplied by  $V_{CE}$ .

- $P_{Q1} = I_{Cmax} \times V_{CE}$ 
  - $I_{Cmax} \approx 5mA$
  - $V_{CEmax} = V_{CC} - V_{R4} = 40V - 5V = 35V$
  - Now make  $V_{CE} = \frac{V_{CEmax}}{2} = \frac{35}{2} = 17.5V$
  - $P_{Q1} = I_{Cmax} \times V_{CE} = 5mA \times 17.5V = 87.5mW$

Calculate  $V_{R3}$  using Kirchhoff's Voltage Law.

- $V_{R3} = V_{CC} - V_{CE} - V_{R4} = 40V - 17.5V - 5V = 17.5V$

Calculate  $I_{R3}$ .

- $I_{R3} \approx 5mA$

Calculate  $R3$  using Ohm's Law.

- $R_3 = \frac{V_{R3}}{I_{R3}} = \frac{17.5V}{5mA} = 3.5K\Omega$

Figure 5-3 displays the regulation circuit with standard values. Figure 5-4 shows the entire rectification circuit with voltage regulation added. Notice the second 10uF capacitor C2 at the base of the transistor. This is used to keep the voltage and current at the base of the transistor extra stable. Figure 5-4 transistor orientation is also drawn in the more typical manner for a power supply.

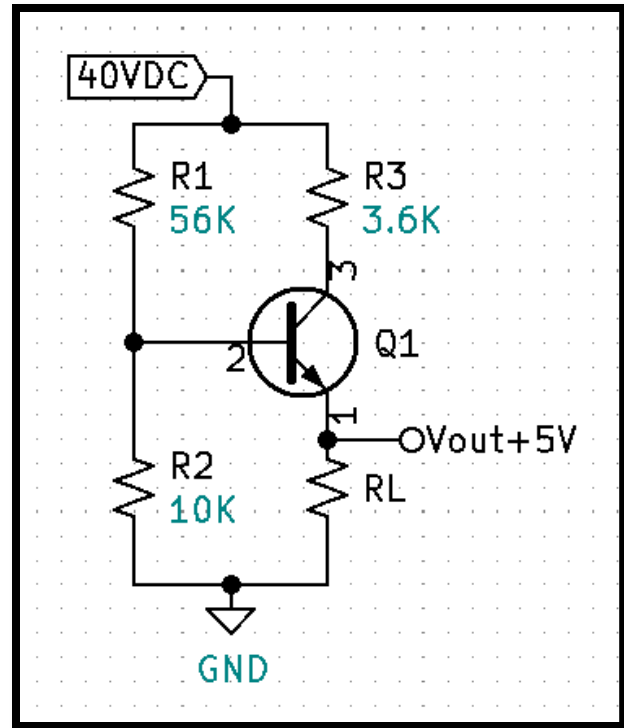


Figure 5-3 Basic Regulation Circuit with Standard Values.

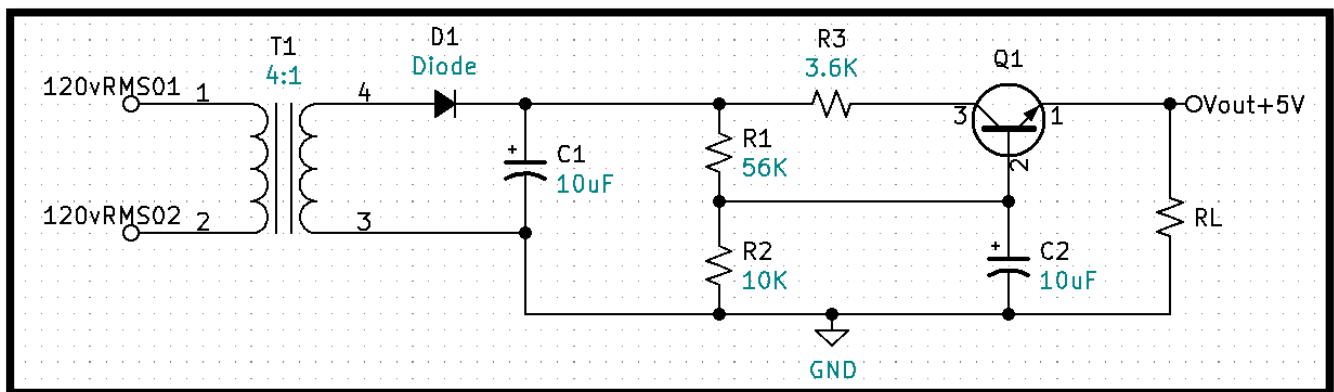


Figure 5-4 Basic Rectification Circuit with Voltage Regulation

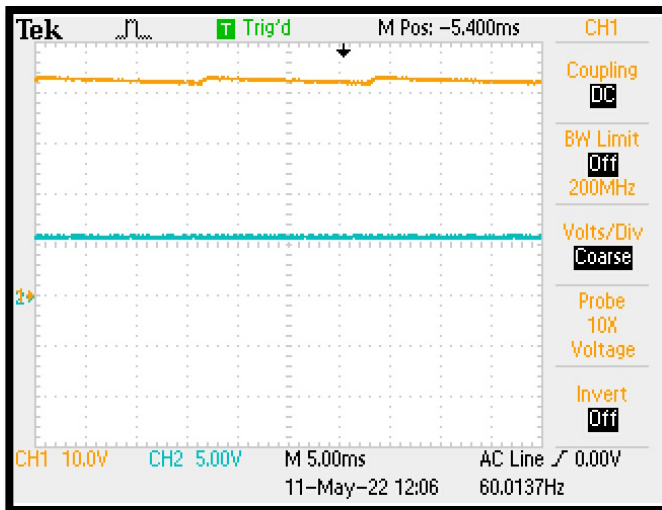


Figure 5-5 CH2 regulated Vout, no load

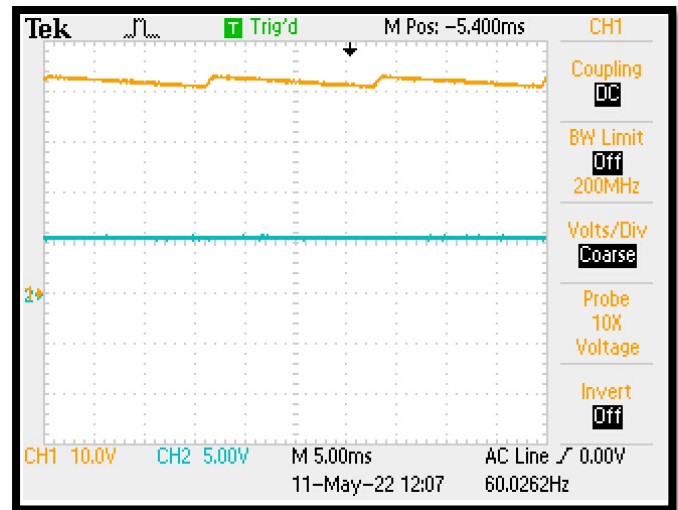


Figure 5-6 CH2 regulated Vout, 10K ohm load

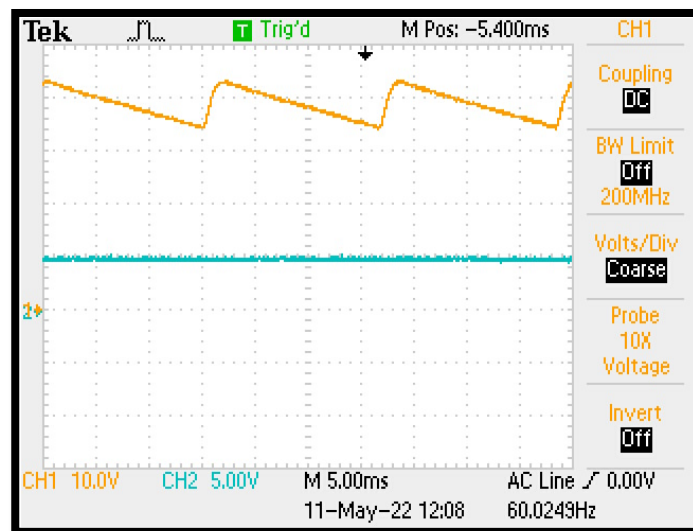


Figure 5-7 CH2 regulated Vout, 1K ohm load

Observe Figure 5-5, 5-6, & 5-7. CH1 is the rectified input voltage across capacitor C1. CH2 is the regulated output which maintains a consistent DC voltage with no ripple from no load to a 1K $\Omega$  load. If you look closely you can see a very small and tolerable shift in the DC level (approximately 0.5V) from no load to 1k. Now let's practice what we have learned by designing basic 5VDC regulator using a 9VDC battery.

## Section 6 Your First Power Supply Project

We learned previously that the human body skin resistance is around  $1K\Omega$  when wet and  $10K\Omega$  when dry. We also learned that 100mAs of current is potentially lethal. If we use a 9VDC battery as our voltage source, what is the maximum current through wet skin and minimum current through dry skin potential exposure? (use Ohm's Law)

- Wet skin:  $I_{wet} = \frac{V}{R} = \frac{9V}{1K\Omega} = 9mA$
- Dry skin:  $I_{dry} = \frac{V}{R} = \frac{9V}{10K\Omega} = 900\mu A$

With dry skin you will not be able to feel or perceive the less than 1mA of current from a 9V battery. If wet however, you could potentially feel a non-lethal shock. Additionally, remove all metal jewelry prior to working with any electronics. Metal jewelry can cause severe burns even when working with low voltage.

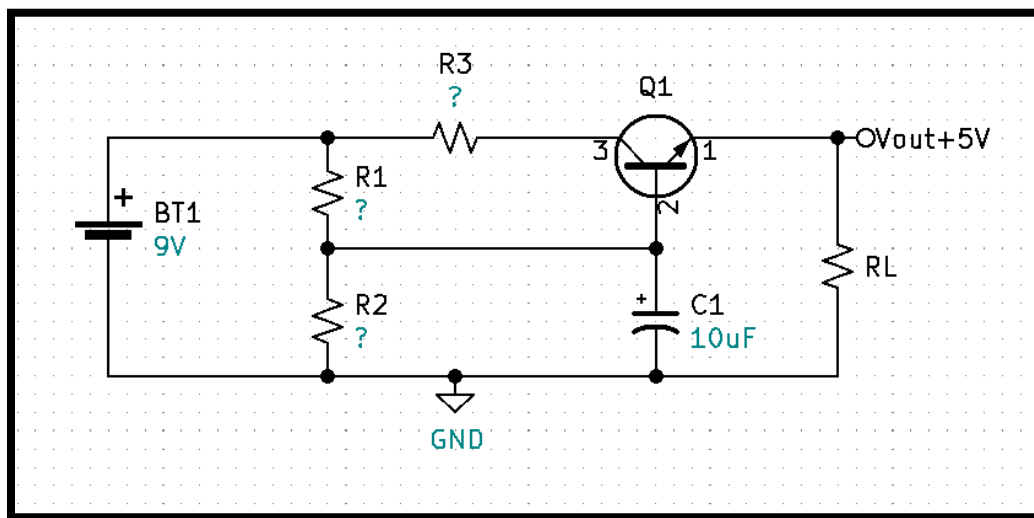


Figure 6-1 5V regulator using a 9V source

**First Challenge:** Calculate and find the resistor values for the circuit in Figure 6-1 to produce a regulated 5V output with a max current of 5mA, assume Q1 is a 2N3904 with a minimum beta of 90.

### Solution for First Challenge:

Find the maximum base current  $I_B$  for Q1.

- $I_{Bmax} \approx \frac{I_{Emax}}{\beta_{min}} \approx \frac{5mA}{90} \approx 55.556\mu A$

Make  $I_{R2} \geq 10 \times I_{Bmax}$ .

- $I_{R2} \geq 10 \times 55.556\mu A \geq 555.556\mu A$

Find  $V_{R2}$  using Kirchhoff's Voltage Law.

- $V_{R2} = V_{BE} + V_{RL} = 0.7V + 5V = 5.7V$

Find approximate  $R_2$  value using Ohm's Law.

- $R_2 \leq \frac{V_{R2}}{I_{R2}} \leq \frac{5.7V}{555.556\mu A} \leq 10.26K\Omega$

Round  $R_2$  value down to a standard value.

- $R_2 = 10K\Omega$

Recalculate  $I_{R2}$  using Ohm's Law.

- $I_{R2} = \frac{V_{R2}}{R_2} = \frac{5.7V}{10K\Omega} = 570\mu A$

Find  $I_{R1}$  using Kirchhoff's Current Law.

- $I_{R1} = I_{R2} + I_B = 570\mu A + 55.556\mu A = 625.556\mu A$

Find  $V_{R1}$  using Kirchhoff's Voltage Law.

- $V_{R1} = V_{BT1} - V_{R2} = 9V - 5.7V = 3.3V$

Calculate  $R_1$  using Ohm's Law.

- $R_1 = \frac{V_{R1}}{I_{R1}} = \frac{3.3V}{625.556\mu A} = 5.28K\Omega$



Determine R3. First ask yourself what the total power of Q1 is without R3 and if that power needs to be split?

- $P_{Q1} = I_{Cmax} \times VCE$ 
  - $V_{CEmax} = V_{BT1} - V_{RL} = 9V - 5V = 4V$
  - $I_{Cmax} = 5mA$
- $P_{Q1} = I_{Cmax} \times VCE = 5mA \times 4V = 20mW$

The absolute maximum power rating for a 2N3904 is 625mW. Optimal power operation for the 2N3904 will be less than or equal to half the absolute maximum rating, approximately 300mW. Because we are well below the optimal power operation at 20mW, R3 is not required for this circuit.

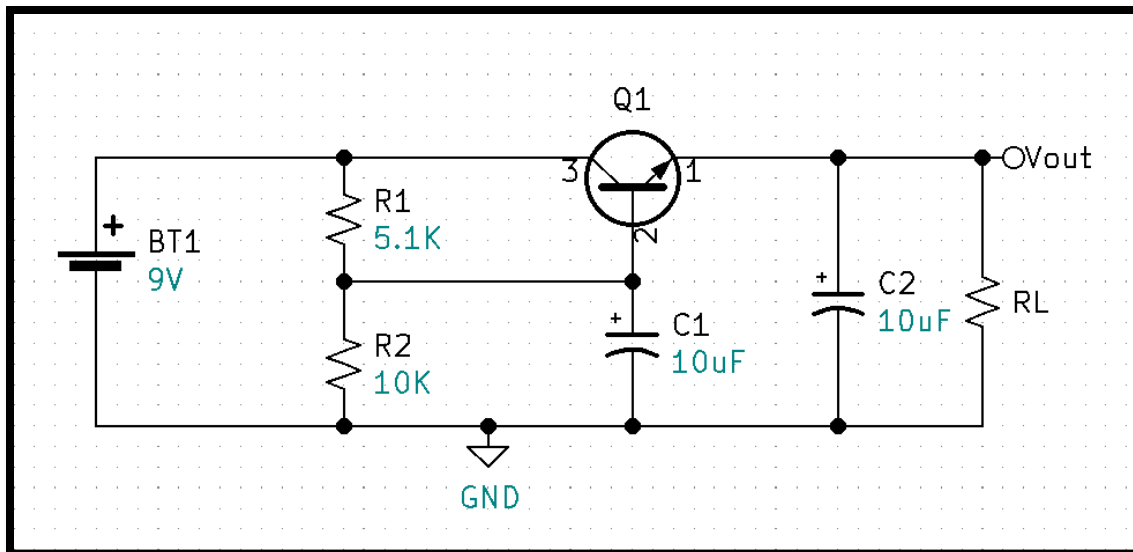


Figure 6-2 Test Circuit - R1 Standard Value, Additional Filter Cap C2.

With figure 6-2 assembled and tested, the output measured a smooth 5.04V with a 1KΩ load resistor and 5.44V with no load. This circuit works good for a specific input voltage, in this case 9VDC. Let's say we want to design a circuit that has the ability to accept a variety of input voltages instead of just 9V. How might we deal with a range of input voltages and still maintain a regulated output of 5V?

## Section 7 Zener Regulation

If you are like me, you have a box full of salvaged electronic components. I have one dedicated to wall ACDC power adapters as seen in Fig. 7-1. These wall adapters, sometimes referred to as “wall warts” take care of voltage rectification for us by internally converting the 120Vrms AC voltage to a fixed DC voltage. Typically, the output voltage and current specifications are written on the adapter. The adapter in Fig 7-1 is listed as having an output of 10.5V that can supply up to 900mAs of current. Let’s say I also have a wall adapter that has a 12V output and third that has a 20V output. Can we design a single circuit that will accommodate each of those inputs and still provide a regulated 5V output? By replacing R2 in our previous circuit with a Zener diode we can achieve regulation throughout a range of input voltages.



Figure 7-1 AC to DC wall power adapter with barrel jack connector

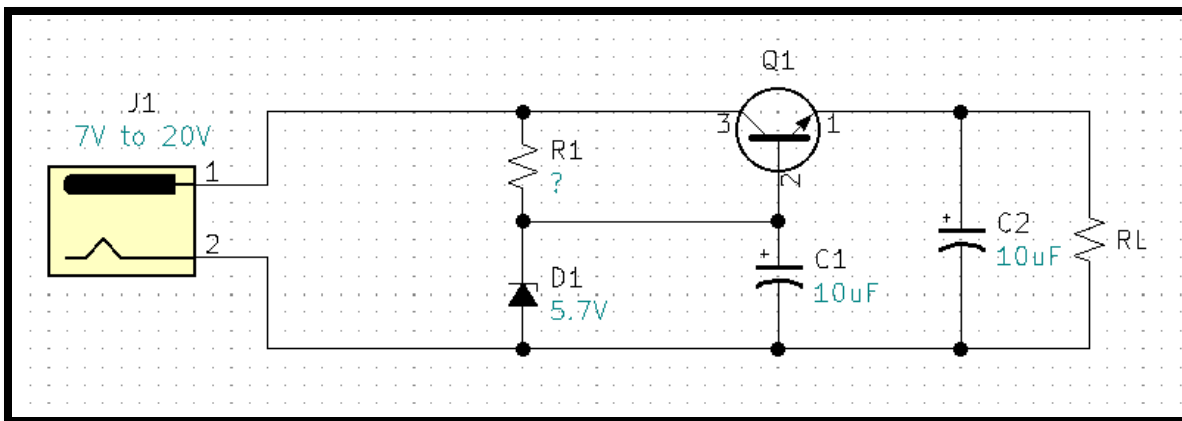


Figure 7-2 Zener regulation circuit with barrel jack input

R1 Calculations for Fig 7-2:

Ideally D1 would be a 5.7V Zener,  
I had on hand a 1N5233 6V Zener diode.  
Concerning Zener diodes, there are two  
important specifications we need to know,  
the maximum Zener current ( $I_{ZM}$ ) and the  
minimum Zener current known as knee  
current ( $I_{ZK}$ ). According to the data sheet  
the maximum power for my Zener is

500mW. With this information we can calculate  $I_{ZM}$ .

Calculate  $I_{ZM}$  using the power formula.

- $P = I \times V$
- $I = \frac{P}{V}$
- $I_{ZM} = \frac{P_{ZMax}}{V_Z} = \frac{500mW}{6V} = 83.333mA$

ABSOLUTE MAXIMUM RATINGS (Note 1)			
Values are at $T_A = 25^\circ\text{C}$ unless otherwise noted.			
Symbol	Parameter	Value	Unit
$P_D$	Power Dissipation	500	mW
	Derate above $50^\circ\text{C}$	4.0	mW/ $^\circ\text{C}$
$T_{STG}$	Storage Temperature Range	-65 to +200	$^\circ\text{C}$
$T_J$	Operating Junction Temperature Range	-65 to +200	$^\circ\text{C}$
	Lead Temperature (1/16 inch from case for 10s)	+230	$^\circ\text{C}$

Stresses exceeding those listed in the Maximum Ratings table may damage the device. If any of these limits are exceeded, device functionality should not be assumed, damage may occur and reliability may be affected.

1. These ratings are limiting values above which the serviceability of any semiconductor device may be impaired.

Non-recurrent square wave Pulse Width = 8.3 ms,  $T_A = 50^\circ\text{C}$ .

Figure 7-3 Data Sheet Excerpt for 1N5233

ELECTRICAL CHARACTERISTICS Values are at $T_A = 25^\circ\text{C}$ unless otherwise noted.										
Device	$V_Z$ (V) @ $I_Z$ (Note 2)			$Z_Z$ ( $\Omega$ ) @ $I_Z$ (mA)		$Z_{ZK}$ ( $\Omega$ ) @ $I_{ZK}$ (mA)		$I_R$ ( $\mu\text{A}$ ) @ $V_R$ (V)		$T_C$ ( $^\circ\text{C}$ )
	Min.	Typ.	Max.							
1N5221B	2.280	2.4	2.52	30	20	1,200	0.25	100	1.0	-0.085
1N5222B	2.375	2.5	2.625	30	20	1,250	0.25	100	1.0	-0.085
1N5223B	2.565	2.7	2.835	30	20	1,300	0.25	75	1.0	-0.080
1N5225B	2.850	3.0	3.150	29	20	1,600	0.25	50	1.0	-0.075
1N5226B	3.135	3.3	3.465	28	20	1,600	0.25	25	1.0	-0.070
1N5227B	3.420	3.6	3.780	24	20	1,700	0.25	15	1.0	-0.065
1N5228B	3.705	3.9	4.095	23	20	1,900	0.25	10	1.0	-0.060
1N5229B	4.085	4.3	4.515	22	20	2,000	0.25	5.0	1.0	$\pm 0.055$
1N5230B	4.465	4.7	4.935	19	20	1,900	0.25	5.0	2.0	$\pm 0.030$
1N5231B	4.845	5.1	5.355	17	20	1,600	0.25	5.0	2.0	$\pm 0.030$
1N5232B	5.320	5.6	5.880	11	20	1,600	0.25	5.0	3.0	0.038
1N5233B	5.700	6.0	6.300	7	20	1,600	0.25	5.0	3.5	0.038
1N5234B	5.890	6.2	6.510	7	20	1,000	0.25	5.0	4.0	0.045

Figure 7-4 Data Sheet IZK

According to the data sheet  $I_{ZK} = 0.25mA$  for the 1N5233 Zener diode.

You can determine your minimum input voltage by adding a minimum of two volts to your regulated output voltage. This extra voltage is needed for the linear regulator to have at least two volts VCE across the transistor. The transistor will lose regulation if its VCE drops too low. For our example with a 5V output we would need a minimum of 7VDC for an input. Now imagine that the input is 7V and the 6V Zener is doing its job. Using Kirchhoff's Voltage Law, we can see that VR1 will equal 1V. Here is the math.

With the input Voltage set to 7V:

- $V_{R1} = V_{in} - V_Z = 7V - 6V = 1V$

We know that the Zener requires a minimum current of  $I_{ZK}$  therefore:

- $R_1 = \frac{V_{R1}}{I_{ZK}} = \frac{1V}{0.25mA} = 4K\Omega$ , round down to next standard value of  $3.9K\Omega$

With the maximum input voltage of 20V chosen, verify  $I_Z$  does not exceed  $I_{ZM} = 83.333mA$ .

With the input Voltage set to 20V:

- $V_{R1} = V_{in} - V_Z = 20V - 6V = 14V$
- $I_Z = \frac{V_{R1}}{R_1} = \frac{14V}{3.9K\Omega} = 3.59mA$
- $I_Z$  is less than  $I_{ZM}$ , and within specifications.

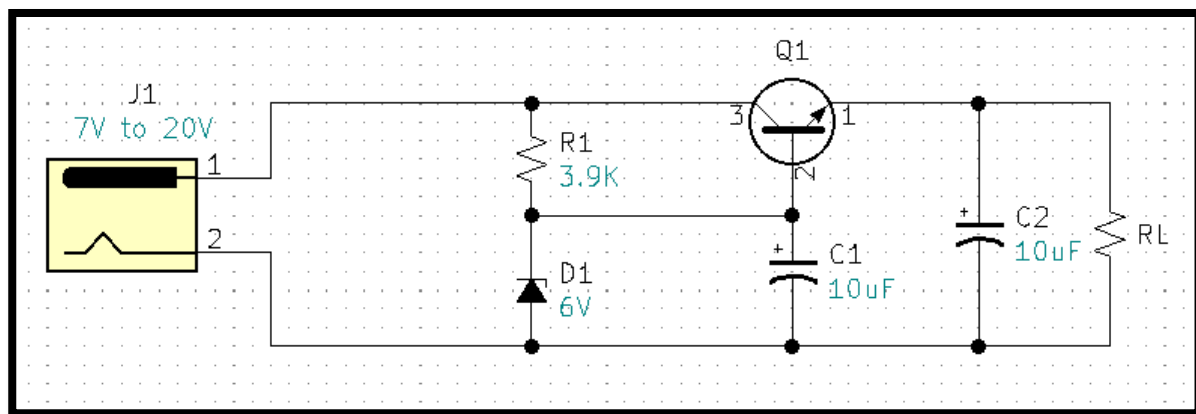


Figure 7-5 Zener Regulated Circuit

One more calculation that should be verified is the power of Q1 when the input is at max 20V.

- $P_{Q1} = I_{RLmax} \times V_{CE}$ 
  - $I_{RLmax} = 5mA$
  - $V_{CEmax} = V_{INmax} - V_{RL} = 20V - 5V = 15V$
- $P_{Q1} = I_{RLmax} \times V_{CE} = 5mA \times 15V = 75mW$
- $P_{Q1} = 75mW$  is less the maximum power for a 2N3904,  $P_{Max2N3904} = 625mW$

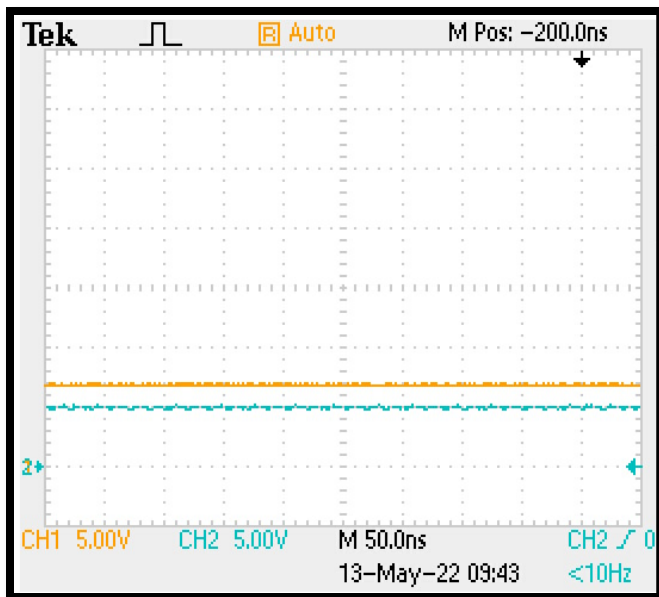


Figure 7-6 Measured, Ch1 7V input & Ch2 5V output.

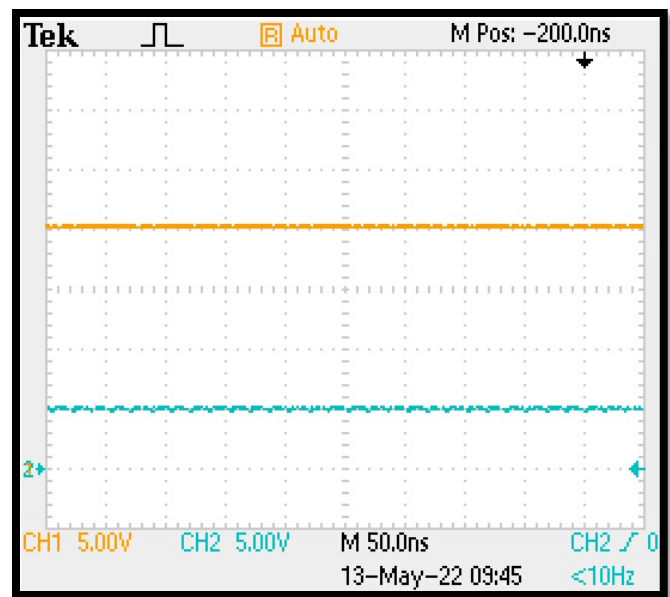


Figure 7-7 Measured, Ch1 20V input & Ch2 5V output.

With Zener regulation we can now regulate a range of input voltages. But only barrel jack connectors that have a

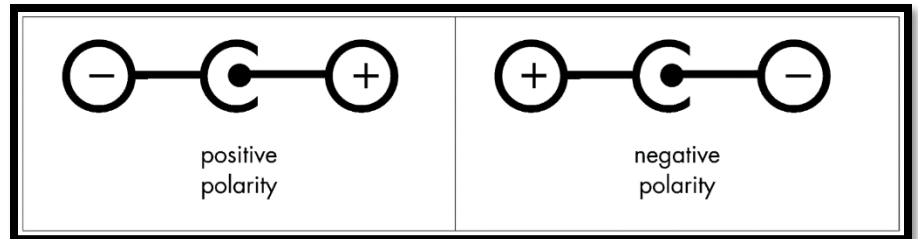


Figure 7-8 Barrel Jack polarity markings

Have you ever noticed the symbol markings on your AC wall adapters similar to Fig 7-8? In my box of salvaged adapters, I have some unmarked, some center positive, and some center negative. Currently, we could damage our circuit, or the wall adapter, if we used

unmarked or center negative adapters. How could our circuit be fixed so that it could accept both positive and negative center pin polarities and still output a fixed +5V?

## Section 8 Input Polarity Correction

Similar to how we used diodes in our AC to DC voltage rectification circuit, we can use diodes to provide DC polarity correction. For this example, I am using 1N4001 general purpose diodes for D1-D4.

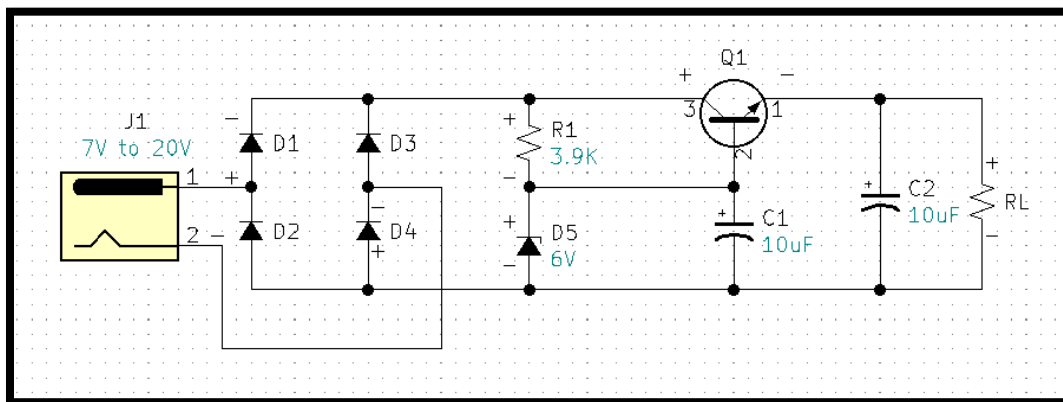


Figure 8-1 Input Polarity Correction, J1 Pin1 Positive.

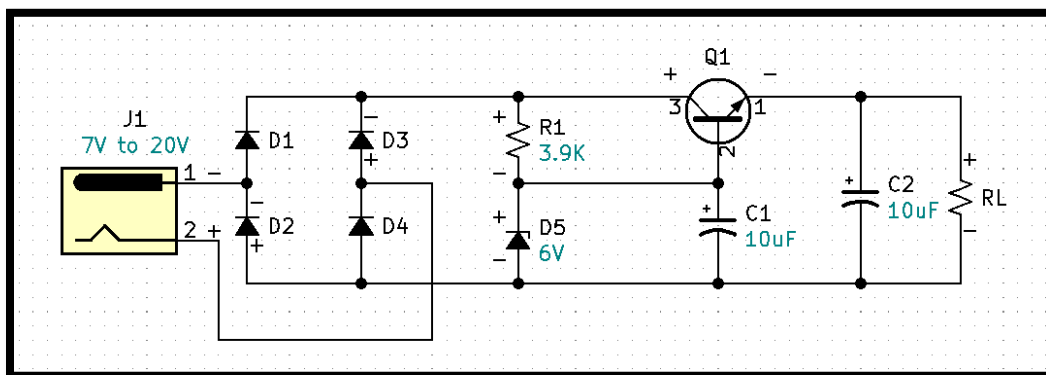


Figure 8-2 Input Polarity Correction, J1 Pin1 Negative.

Observe Figure 8-1 where J1 pin 1 is positive with respect to pin 2, diodes D1 and D4 are forward biased and diodes D2 and D3 are reverse biased. The result is the rest of the circuit is properly biased. Observe Figure 8-2 where J1 pin 1 is negative with respect to pin 2, diodes D2 and D3 are forward biased and diodes D1 and D4 are reverse biased. The result is the rest of the

circuit is again properly biased. Therefore, the circuit is now adapted to receive either positive, negative, or unknown voltage polarities. This circuit makes virtually all of our salvaged wall adapters useable. I assembled and tested the circuit with +20VDC input measured +5.08VDC at the output with a 1K $\Omega$  load. I also tested with -20VDC input and also measured +5.08VDC at the output with a 1K $\Omega$  load.

What happens to this circuit if the output is shorted? The answer is the transistor will exceed its power specifications and destroy itself. None of the previous circuits have had current limiting protection. If you are building a dedicated circuit that will be deployed with a fixed load and a fixed input voltage, and you can guarantee that the output will never be shorted, the previous circuits may work fine. However, current limiting circuit protection is always a good idea. What is a simple way to apply current limiting protection to our circuit?

## Section 9 Basic Current Limiting Protection

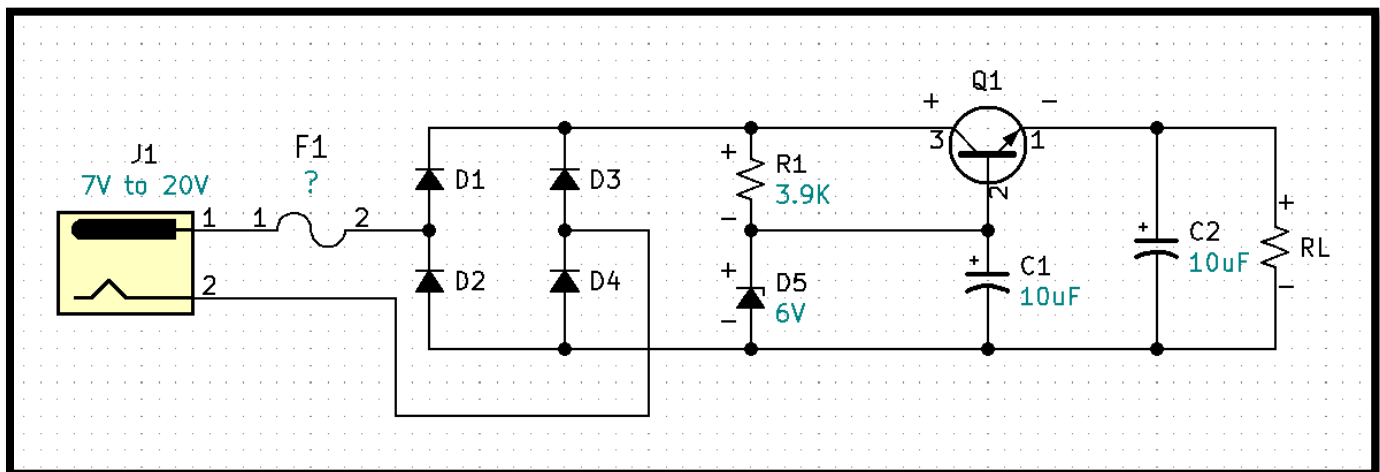


Figure 9-1 Simple current limiting protection provided by F1 fuse.

A fuse can provide basic current limiting protection for your circuit. To determine the proper fuse value, we need to consider all the parts that will be affected when the output is shorted or overloaded. We can see that Q1 and the polarity correction diodes are in the direct



path between the voltage source and the output. Additionally, we should consider the output rating on the AC/DC wall adapter. All wall adapters will be rated differently. As previously mentioned, my adapter is rated at 900mA. According to the data sheet the 1N4001 diodes are rated at a maximum forward current of 1A. And the 2N3904 BJT is rated at an absolute maximum forward DC current of 200mA. So, for this circuit we will need to protect the weakest link which is the 2N3904 BJT at 200mA. If your wall adapter is rated less than 200mA, your fuse choice would be based on that current. Because 200mA is the absolute maximum, we will want to guarantee that the current stays well below 200mA. Our circuit is designed to run at 5mA so our fuse will need to be larger than 5mA and well below 200mA. An appropriate fuse for this circuit is a slow blow 100mA or 0.1A fuse.

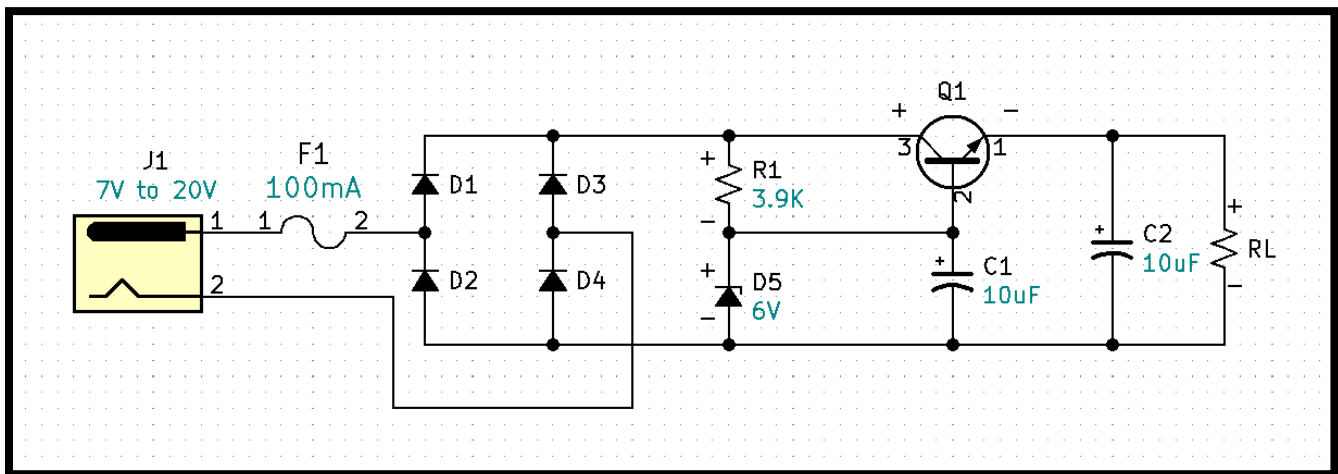


Figure 9-2 Fuse F1 = 100mA or 0.1A

We know the transistor Q1 can handle a forward current of 100mA. We need to recalculate the transistors power with a load current of 100mA and determine if the power at Q1 is still in specification.

New Calculations:

- $$R_{L@100mA} = \frac{V_{RL}}{I_{RL}} = \frac{5V}{100mA} = 50\Omega$$

- $P_{Q1@100mA} = V_{CEmax} \times I_{Cmax}$ 
  - $V_{CEmax} = V_{INmax} - V_{RL} = 20V - 5V = 15V$
  - $I_{Cmax} = F1 = 100mA$
- $P_{Q1@100mA} = V_{CEmax} \times I_{Cmax} = 15V \times 100mA = 1.5 \text{ watts}$

$P_{Q1}$  at 1.5 watts is too high for the 2N3904. There are two ways we can deal with this problem. The first is to do a power split by adding a series parasitic power resistor in the path of the collector of the transistor just like we did previously with R3 in the rectifying circuit Fig. 5-1. The second option is to use a Darlington Pair.

First let's calculate the parasitic power resistor.

- $P_{total} = 1.5 \text{ watts}$ 
  - $P_{Q1max} = 625mW$
  - $P_{R2max} = P_{total} - P_{Q1max} = 1.5 \text{ watts} - 625mW = 875mW$
- $V_{R2} = \frac{P_{R2max}}{I_{Cmax}} = \frac{875mW}{100mA} = 8.75V$
- $R_2 = \frac{V_{R2}}{I_{Cmac}} = \frac{8.75V}{100mA} = 87.5\Omega$

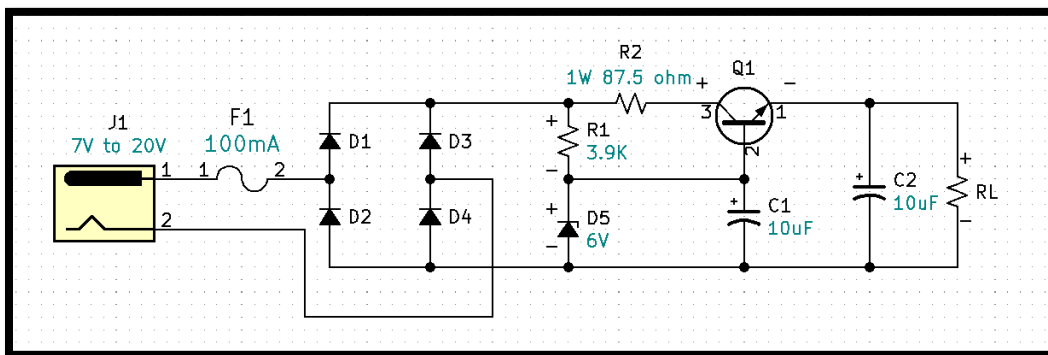


Figure 9-3 Parasitic R2 power protection for Q1

The circuit Fig 9-3 will work fine when the load is 5mA. However, now that we can operate up to 100mA without damaging any of the parts, a problem has been introduced via R2.

Can you spot the problem? If we want to operate our output at 99mA, what is the required input voltage for Fig 9-3?

Calculate the required input voltage when the output is running a 99mA load.

- $V_{in} = V_{D1} + V_{D4} + V_{R2} + V_{CE} + V_{RL}$ 
  - $V_{D1\&D4} = 0.7V$
  - $V_{R2} = I_C \times R_2 = 99mA \times 87.5 = 8.663V$
  - $V_{CEmin} = 2V$
  - $V_{RL} = 5V$
- $V_{in} = 0.7 + 0.7 + 8.663 + 2V + 5V = 17.063V$ 
  - $V_{in} = 17.063V$

A  $V_{in}$  requirement of 17V for our circuit is not practical. Using this method would severely limit the flexibility of this circuit. A preferable method is to use a Darlington Pair with a higher-powered transistor.

## Section 10 The Darlington Pair

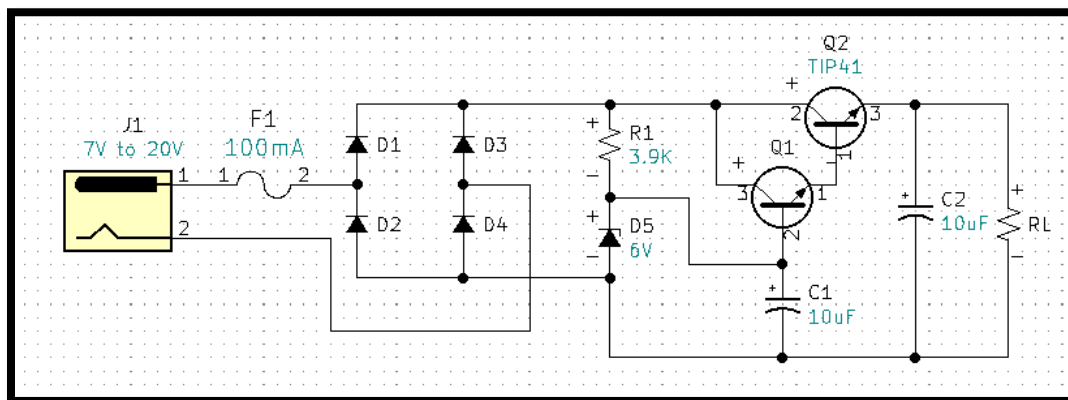


Figure 10-1 5V Regulator with Darlington Pair.

The Darlington Pair Q1 & Q2 is a current multiplier. The power transistor TIP 41 is able to handle more power than the 2N3904. Here is a question you may be thinking, why not omit the 2N3904 Q1 transistor and replace it with the power transistor TIP41? The answer is, power

transistors have a much lower beta or hfe than general purpose transistors. Therefore, our base current would go up significantly and we would still need 10X current through the Zener. We would also need to keep our IZ current below IZM. Additionally, the increase in IZ would require a recalculation of the R1 value to accommodate the increase in current. This would negatively impact our efficiency, we don't want more quiescent current to go directly to ground through the Zener. Imagine if your power supply was battery powered, an increase in IZ would discharge your battery faster. By adding the Darlington, we can keep the current through the Zener significantly lower, while increasing the current through the load. With the Darlington Pair, if the circuit was run at its maximum current of 100mA, what would the current at the base of Q1 be?

- $R_L = \frac{V}{I} = \frac{5V}{100mA} = 50\Omega$ :
- $I_{RL} = \frac{V_{RL}}{R_L} = \frac{5V}{50\Omega} = 100mA$
- $I_{EQ2} = I_{RL} = 100mA$
- $I_{BQ2} \approx \frac{I_{EQ2}}{TIP41\beta_{min}} \approx \frac{100mA}{?}$  (see fig 36 for beta/hfe min)
- $I_{BQ2} \approx \frac{100mA}{20} \approx 5mA$
- $I_{EQ1} \approx I_{BQ2} \approx 5mA$
- $I_{BQ1} \approx \frac{I_{EQ1}}{2N3904\beta_{min}} \approx \frac{5mA}{90}$
- $I_{BQ1} \approx \frac{I_{EQ1}}{2N3904\beta_{min}} \approx 55.556\mu A$

TIP41, TIP41A, TIP41B, TIP41C (NPN); TIP42, TIP42A, TIP42B, TIP42C (PNP)					
ELECTRICAL CHARACTERISTICS (T <sub>C</sub> = 25°C unless otherwise noted)					
Characteristic	Symbol	Min	Max	Unit	
<b>OFF CHARACTERISTICS</b>					
Collector-Emitter Sustaining Voltage (Note 2) (I <sub>C</sub> = 30 mA, I <sub>B</sub> = 0)	TIP41, TIP42 TIP41A, TIP42A TIP41B, TIP42B TIP41C, TIP42C	V <sub>CE(sus)</sub>	40 60 80 100	- - - -	V <sub>dc</sub>
Collector Cutoff Current (V <sub>CE</sub> = 30 Vdc, I <sub>B</sub> = 0) (V <sub>CE</sub> = 60 Vdc, I <sub>B</sub> = 0)	TIP41, TIP41A, TIP42, TIP42A TIP41B, TIP41C, TIP42B, TIP42C	I <sub>CEO</sub>	- -	0.7 0.7	mA <sub>dc</sub>
Collector Cutoff Current (V <sub>CE</sub> = 40 Vdc, V <sub>EB</sub> = 0) (V <sub>CE</sub> = 60 Vdc, V <sub>EB</sub> = 0) (V <sub>CE</sub> = 80 Vdc, V <sub>EB</sub> = 0) (V <sub>CE</sub> = 100 Vdc, V <sub>EB</sub> = 0)	TIP41, TIP42 TIP41A, TIP42A TIP41B, TIP42B TIP41C, TIP42C	I <sub>CES</sub>	- - - -	400 400 400 400	μA <sub>dc</sub>
Emitter Cutoff Current (V <sub>BE</sub> = 5.0 Vdc, I <sub>C</sub> = 0)		I <sub>EBO</sub>	-	1.0	mA <sub>dc</sub>
<b>ON CHARACTERISTICS (Note 2)</b>					
DC Current Gain (I <sub>C</sub> = 0.3 Adc, V <sub>CE</sub> = 4.0 Vdc) (I <sub>C</sub> = 3.0 Adc, V <sub>CE</sub> = 4.0 Vdc)		h <sub>FE</sub>	30 15	- 75	-
Collector-Emitter Saturation Voltage (I <sub>C</sub> = 6.0 Adc, I <sub>B</sub> = 600 mA <sub>dc</sub> )		V <sub>CE(sat)</sub>	-	1.5	V <sub>dc</sub>
Base-Emitter On Voltage (I <sub>C</sub> = 6.0 Adc, V <sub>CE</sub> = 4.0 Vdc)		V <sub>BE(on)</sub>	-	2.0	V <sub>dc</sub>
<b>DYNAMIC CHARACTERISTICS</b>					
Current-Gain — Bandwidth Product (I <sub>C</sub> = 500 mA <sub>dc</sub> , V <sub>CE</sub> = 10 Vdc, f <sub>test</sub> = 1.0 MHz)		f <sub>T</sub>	3.0	-	MHz
Small-Signal Current Gain (I <sub>C</sub> = 0.5 Adc, V <sub>CE</sub> = 10 Vdc, f = 1.0 kHz)		h <sub>ie</sub>	20	-	-

Figure 10-2 Beta for a TIP41 transistor.

Note, our output prior to the Darlington Pair was designed for a maximum 5mA, we decided to increased output load capability to 100mA. This is a current gain or increase of 20. Adding the Darlington pair with a TIP41 power transistor solved two problems. The first was the TIP can handle the increased circuit power and the second the TIP41 with its minimum beta of 20 gave the Darlington a current magnification factor of 20, keeping the base current of Q1 and IZ the same which allows R1 to remain the same.

I assembled and tested the regulator circuit fig 10-1. The circuit was tested with 20V & 7V inputs and with 1K $\Omega$  & 50 $\Omega$  loads. The circuit performed as expected with a regulated output of 5V for each scenario. This circuit works great however, we should consider the limitations and associated cost. For Q2 any power over two watts will require the TIP41 have a heat sink. A heat sink is a relatively expensive component. The TIP41 cost itself is just under a dollar. The Zener diode, the fuse and a fuse holder also add cost. Is there a single component that could replace the fuse, fuse holder, Zener diode, and both Bipolar Junction Transistors?

We can purchase an off the shelf, dedicated, all in one 5V (and other standard value) linear voltage regulators for less than a dollar!

## **Section 11 The L7805 Regulator**

The L7805 is a 5V fixed linear regulator with internal current limiting and built-in temperature protection. The L7805 is part of the L78 series of linear regulators. The L78 series can be purchased as 5V, 6V, 8V, 8.5V, 9V, 12V, 15V, 18V, and 24V regulators. One point to understand is linear regulators can only regulate down, they cannot regulate up. For the L7805 5V regulator the input voltage can be minimum of 6V to an absolute maximum voltage of 35V. At the time of writing this document I can purchase a single L7805 for \$0.62.

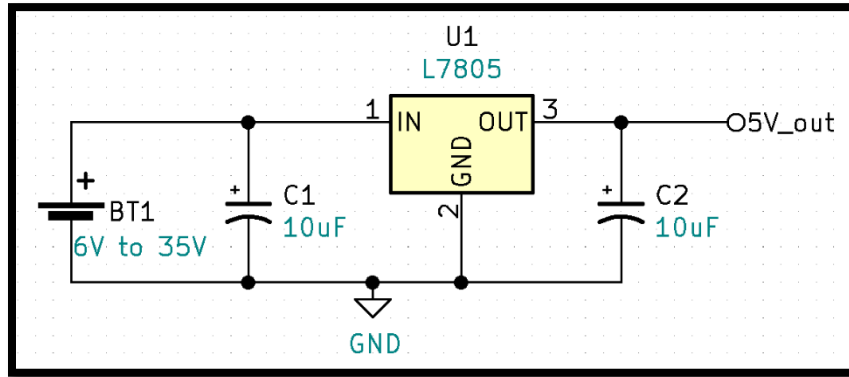


Figure 11-1 L7805 Linear 5V Regulator basic test circuit

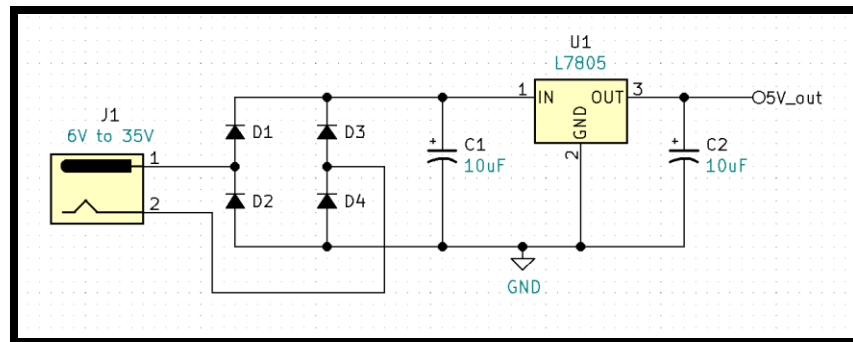


Figure 11-2 L7805 Linear 5V Regulator with Barrel Jack input and Polarity Correction

Notice that in Fig 11-1 circuit the fuse has been removed. This is because the L7805 has internal current limiting and over temperature protection which will provide adequate protection for the circuit. Fig 11-2, Diodes D1 – D4 provide polarity correction, ensuring that pin1 of the L7805 is always positive.

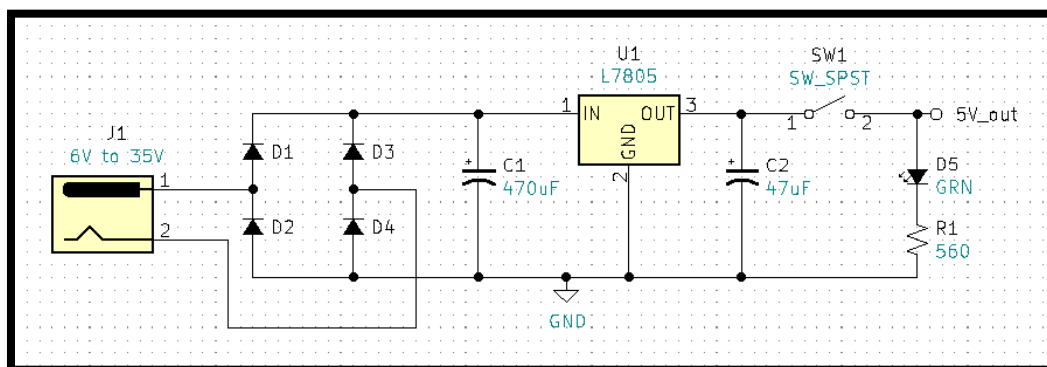


Figure 11-3 Final circuit with SW1 and power indication

Figure 11-3 is the final circuit. The capacitor values are increased for additional filtering. SW1 was added for switchable output voltage. The logical position for this SW1 would have

been at the input. However, this project has a small size or form factor and the micro switch is used is rated at 6V, so the problem with putting the switch in series with J1 is that it would be out of specification due to overvoltage. The problem with SW1 current position is the quiescent current of the L7805. Linear Regulators are inefficient when compared to Switch Mode Power Supplies. The inefficiency of the L7805 is due to the fact that the regulator requires a certain amount of current to operate even if there is no load at the output. This would be comparable to the Zener current in the previous circuits. This current is called Quiescent Current and the typical quiescent current, per the data sheet, for a L7805 is 3.2mA. If you are using a 9V battery and a barrel adapter to power your breadboard power supply circuit you will need to unplug the barrel jack after testing to ensure the battery does not drain down. The typical 9V battery is rated at 500mAh, meaning if you run the battery at 500mAs, it will be drained in one hour. So, if our linear regulator requires 3.2mAs and we have no load (no current) at the output, how long will it take to drain the 9V battery?

- $500mA = 1hour, 3.2mA = x \text{ hours?}$

- $x = \frac{500mA \times 1hour}{3.2mA} = 156.25 \text{ hours}$

If you leave your 9V battery plugged into the breadboard power supply with no load at the output, you will have a dead battery after 156 hours. I considered not having a switch at all, making the circuit even simpler, and forcing the operator plug and unplug the barrel jack.

However, I like having the ability to switch on and off the 5V GND rails on the breadboard and the goal of this project was to be able to use salvaged barrel jack ACDC wall adapters.

The green LED D5 provides on/off output indication. The maximum current rating for the LED is 30mA. The forward voltage for this green LED is approximately 2V. This leaves us



with 3V across the current limiting resistor R1. What is the minimum resistance that R1 can be without exceeding the diodes 30mA max current?

$$R1_{min} = \frac{3V}{30mA} = 100\Omega$$

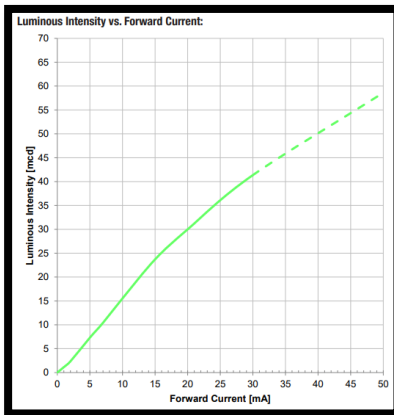


Figure 11-5 LED Intensity vs. Forward Current

As R1's resistance value is increased, the LEDs forward current will decrease, and the

LEDs luminous intensity will decrease. Bench testing found that a 560Ω resistor provides a minimum current with adequate LED illumination.

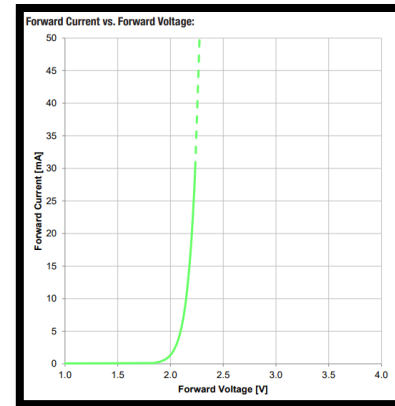


Figure 11-4 LED Forward Current vs. Forward Voltage

## Section 12 Breadboard Power Supply Assembly

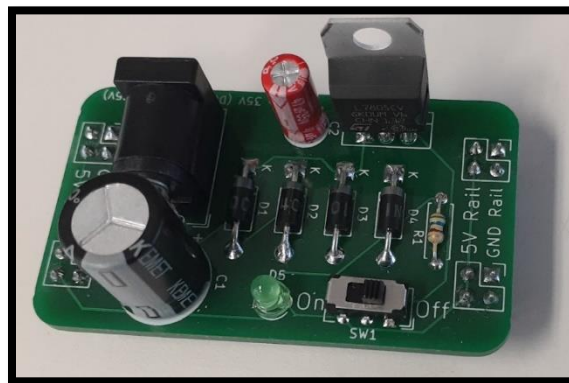


Figure 12-1 Fully Assembled Breadboard Power Supply

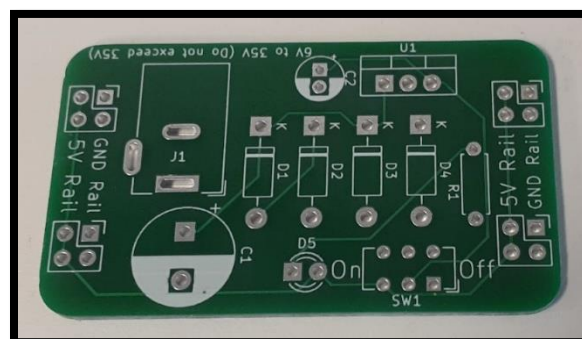


Figure 12-2 PCB with no parts

Start by soldering diodes D1 – D4.

Make sure the orientation is correct, the silver band is the cathode and goes toward the K.

Solder R1, R1s orientation is not important. D5 the LED must be soldered with the proper orientation. There is a flat side on the collar of the LED, this flat side should be associated with the short lead. The short lead and flat side collar should be soldered to the square pad. The long lead of the LED goes to the round pad. The long lead of the LED goes to the round pad, toward SW1.

The electrolytic capacitors are polarity sensitive and must be installed correctly. Solder the negative pins to the round pad with the white and the positive pin to the square pad.

The barrel plug input adapter has kinked pins. At first this part can be a little difficult to get into position. Make sure to align the pins and then press hard and it should snap into place. Orientate the L7805 as seen in the picture, front to the circuit and back to open space.

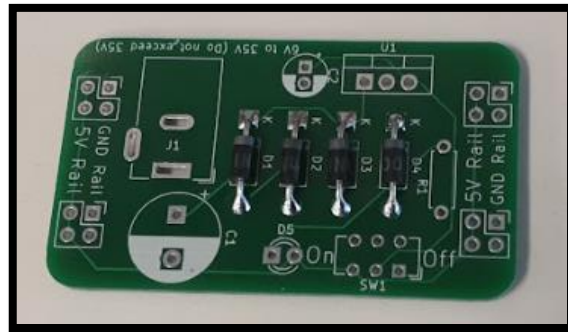


Figure 12-3 Add polarity correction diodes

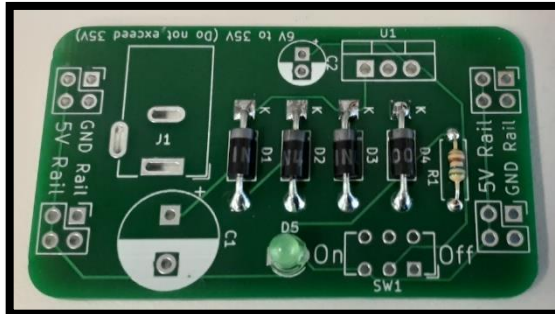


Figure 12-4 Add the power indication circuit, LED & R1



Figure 12-5 Add Filter Capacitors



Figure 12-6 Add Barrel Plug Adapter and the L7805 Regulator

Snap off the header pins in 2x2 groups. The easiest way to do this is to use two needle nose pliers. On the breadboard there five pin groups going down the power rails.

Orientate the header pins as seen in the picture in the first slots of two adjoining five pin groups. Notice the snap off tabs are all orientated in the same direction.

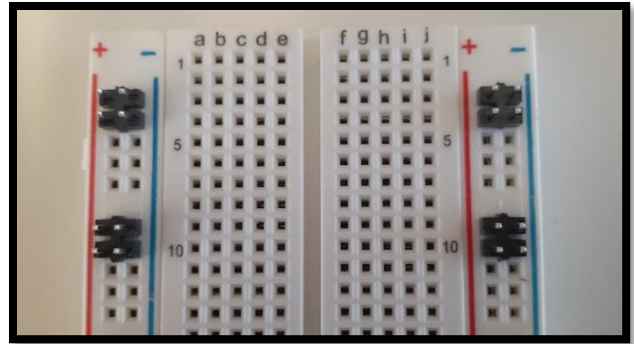


Figure 12-7 Header Pin Alignment to breadboard

Place the PCB on the header pins and press firmly to make sure all the header pins are square and flush to the breadboard. Solder the header pins in

place, from the top of the PCB.

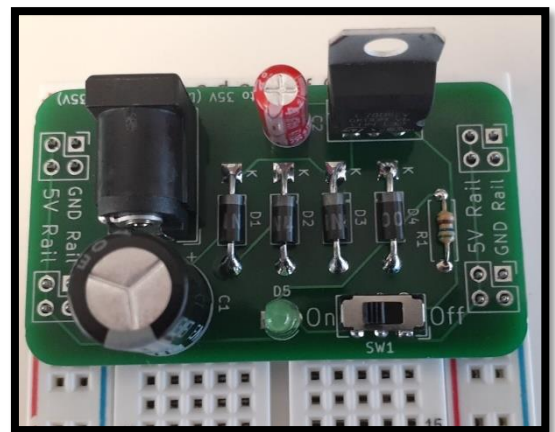


Figure 12-8 Place PCB on header pins.

After soldering the header pins, the Breadboard Power Supply is complete. Plug in your ACDC wall adapter. Test that the green led turns on and off with SW1 and verify that both power rails have 5VDC.

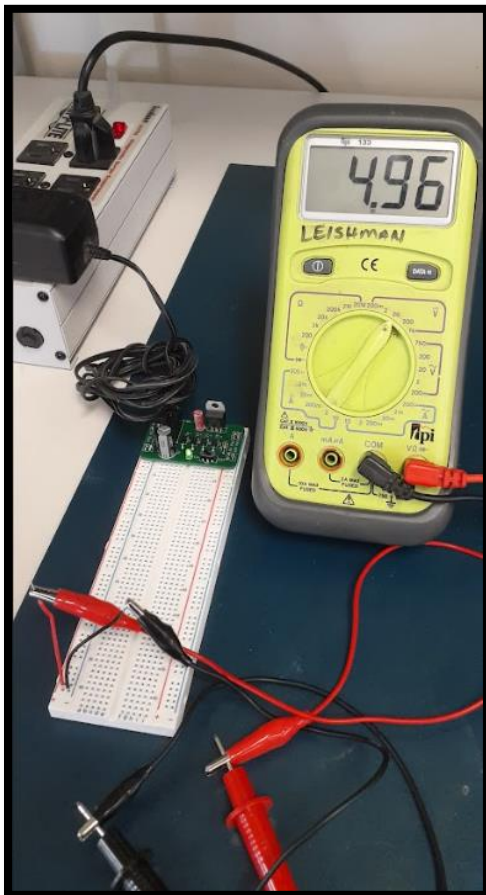


Figure 12-9 Final Test

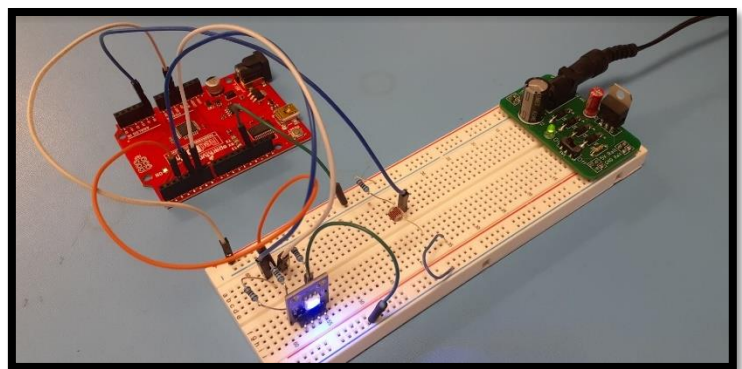


Figure 12-10 Breadboard Power Supply powering an Arduino project.

## Conclusion

I hope you enjoyed this lesson on Linear Regulated Power Supplies. Now put your new Breadboard Power Supply to work and develop lots of cool electronic projects. If you are interested in a career in electronics, consider taking your skills to the next level by studying with me at Idaho State University's Robotics and Communications Systems Engineering Technology program. We are happy to give program tours! So, come check us out. Please contact me at [leistimo@isu.edu](mailto:leistimo@isu.edu).

If you are a Middle School or High School STEM teacher please connect with me and consider purchasing the Breadboard Power Supply kits from the Idaho State University Electronics Club. The proceeds earned from the Breadboard Power Supply kits will help support students at the Skills USA competition and other club events. Please contact me at [leistimo@isu.edu](mailto:leistimo@isu.edu).

## References

- OSHA. (n.d.). *Basic Electricity Safety - Occupational Safety and Health Administration*. Train-the-Trainer: Basic Electrical Safety. Retrieved May 18, 2022, from [https://www.osha.gov/sites/default/files/2019-04/Basic\\_Electricity\\_Materials.pdf](https://www.osha.gov/sites/default/files/2019-04/Basic_Electricity_Materials.pdf)
- ONSEMI. (n.d.). *1N4001 Datasheet*. Digi-Key. Retrieved May 18, 2022, from <https://www.onsemi.com/pdf/datasheet/1n4001-d.pdf>
- STMicroelectronics. (n.d.). *2N3904 Datasheet*. Digi-Key. Retrieved May 18, 2022, from <https://media.digikey.com/pdf/Data%20Sheets/ST%20Microelectronics%20PDFS/2N3904.pdf>
- Portable Powerguides.com. (n.d.). *How Many Amps Is A 9 Volt Battery? (With its Watt & Usage)*. Retrieved May 18, 2022, from <https://portablepowerguides.com/how-many-amps-is-a-9-volt-battery/>
- ON Semiconductor. (n.d.). *Zener Diodes Datasheet*. Digi-Key. Retrieved May 18, 2022, from <https://www.onsemi.com/pdf/datasheet/1n5221b-d.pdf>
- Positive Polarity Negative Polarity Image*. (n.d.). Retrieved May 18, 2022, from <https://i.stack.imgur.com/zsp7C.png>.
- ON Semiconductor. (n.d.). *TIP41 Datasheet*. Digi-Key. Retrieved May 18, 2022, from <https://media.digikey.com/pdf/Data%20Sheets/ON%20Semiconductor%20PDFs/TIP41A-D.pdf>
- STMicroelectronics. (n.d.). *L7805 Datasheet*. Digi-Key. Retrieved May 18, 2022, from <https://www.st.com/content/ccc/resource/technical/document/datasheet/41/4f/b3/b0/12/d4/47/88/CD00000444.pdf/files/CD00000444.pdf/jcr:content/translations/en.CD00000444.pdf>
- DIODES INC. (n.d.). *7805 Datasheet*. Digi-Key. Retrieved May 18, 2022, from <https://www.diodes.com/assets/Datasheets/AS78XXA.pdf>
- WURTH ELEKTRONIK. (n.d.). *LED Datasheet*. Digi-Key. Retrieved May 18, 2022, from <https://www.we-online.com/katalog/datasheet/151031VS06000.pdf>